

Review of Digital Circuits & Logic Design

Number Systems

Common Number Systems

System	Base	Symbols	Used by humans?	Used in computers?
Decimal	10	0, 1, ... 9	Yes	No
Binary	2	0, 1	No	Yes
Octal	8	0, 1, ... 7	No	No
Hexa-decimal	16	0, 1, ... 9, A, B, ... F	No	No

Number Systems


Quantities/Counting

Decimal	Binary	Octal	Hexa-decimal
0	0	0	0
1	1	1	1
2	10	2	2
3	11	3	3
4	100	4	4
5	101	5	5
6	110	6	6
7	111	7	7

Decimal	Binary	Octal	Hexa-decimal
8	1000	10	8
9	1001	11	9
10	1010	12	A
11	1011	13	B
12	1100	14	C
13	1101	15	D
14	1110	16	E
15	1111	17	F

Number Systems

Conversion Among Bases

 

Number Systems

Decimal to Binary

- Technique
 - Divide by two, keep track of the remainder
 - First remainder is bit 0 (LSB, least-significant bit)
 - Second remainder is bit 1, and so on

$$125_{10} = ?_2$$

2		125	
2		62	1
2		31	0
2		15	1
2		7	1
2		3	1
2		1	1
		0	1



$$125_{10} = 1111101_2$$

Number Systems

Hexadecimal to Binary

- Technique
 - Convert each hexadecimal digit to a 4-bit equivalent binary representation

$$10AF_{16} = ?_2$$

1	0	A	F
↓	↓	↓	↓
0001	0000	1010	1111

$$10AF_{16} = 0001000010101111_2$$

- Reverse the process when converting binary to hexadecimal

Number Systems

Negative Numbers

- Two ways to represent a negative binary number.
 - a signed bit to represent the positive or negative sign.
 - the complemented form of the positive number to represent a negative value.
- Negative number represented by a *sign* preceding its absolute value, e.g. -65.
- Similar technique can be employed to represent a negative binary number.
- Attach one digit to the binary number to represent the sign.
- This binary digit is the *sign bit*.
- Sign bit is always the MSB.** The number is positive if the sign bit is 0 and is negative if the sign bit is 1.
- For example, 00101₂ represents +0101₂, while 10101₂ means -0101₂

Number Systems

- The advantage is simple.
- Disadvantages
 - Duplication in representing zero.
 - i.e., 00 and 10 represent zero
 - addition to a signed negative number gives an **incorrect** answer.

+	1011101	(+93)
-	1000001	(-65)
	0011100	(+28)

+	01011101	(+93)
	11000001	(-65)
1	00011110	(+30)
↑		
Overflow		

Number Systems

Complement representation

- The 1's complement and the 2's complement.
- The most significant bit still represents the sign.
- The other digits are not the same.

1's complement

- The negative value of an n-digit binary number, N_2 , can be represented by its 1's complement, N'_2
- It is equal to the base number, 2, to the power n minus the number N minus one, or:
$$N'_2 = 2^n - N_2 - 1 = (2^n - 1) - N_2$$
- N'_2 can be obtained by subtracting each digit with 1, or by inverting all binary digits.

Number Systems

- 1's complement number of **01001101**₂:
- $n = 8$.

$$\begin{aligned} N'_2 &= (2^8 - 1) - N_2 \\ &= (100000000 - 1) - 01001101 \\ &= 11111111 - 01001101 \\ &= 10110010_2 \end{aligned}$$

Number Systems

2's complement

- The 2's complement, N''_2 , of an n-digit binary number, N_2 , is defined as:
$$\begin{aligned} N''_2 &= 2^n - N_2 \\ &= (2^n - 1) - N_2 + 1 \\ &= N'_2 + 1 \end{aligned}$$
- where N'_2 is the 1's complement representation of the number.

Number Systems

- No duplicate representation for all numbers.

$$N_2 = 00000000$$

$$N'_2 = 11111111$$

$$N''_2 = N'_2 + 1 = 1\ 00000000$$

- Since only 8 bits are used, the base complement of zero is zero, too.
- With 8-bit 2's complement representation, total 256 numbers
10000000₂ (-128₁₀) to **00000000**₂ (0₁₀) to **01111111**₂ (+127₁₀).

Number Systems

- 2's complement number of **01001101**.

1's complement, N' is **10110010**

$$\begin{aligned} N'' &= N' + 1 \\ &= 10110010 + 1 \\ &= 10110011 \end{aligned}$$

- Subtraction of two numbers:

$$X_2 - Y_2 = X_2 + (-Y_2)$$

- In 2's complement representation:

$$X_2 + (2^n - Y_2) = X_2 - Y_2 + 2^n$$

- If $X > Y$, the sum will produce an end carry, 2^n , which can be discarded, and the sum is positive.

Number Systems

- If $X < Y$, the sum is negative and will be

$$2^n - (Y_2 - X_2)$$

which is the 2's complement of $(Y_2 - X_2)$.

- Example: $93 - 65$

$$+93 = 01011101_2$$

$$-65 = 100000000 - 01000001 = 10111110 \quad (\text{in 1's complement})$$

$$= 10111111 \quad (\text{in 2's complement})$$

93 - 65			
01011101	(+93)	(X)	
+	10111111	(-65)	(2 ⁸ - Y)
1	00011100	(+28)	(X - Y)
↑			
			Overflow (2 ⁸)

Number Systems

- Example: $65 - 93$

$$+65 = 01000001_2$$

$$-93 = 100000000 - 01011101$$


$$= 10100010 \quad (\text{in 1's complement})$$

$$= 10100011 \quad (\text{in 2's complement})$$

65 - 93			
01000001	(+65)	(X)	
+	10100011	(-93)	(-Y)
1	11000100	(-ve)	
↑			
			2 ⁸ - (Y - X)
1	00000000		2 ⁸
-	11100100	2 ⁸ - (Y - X)	
0	00111100	-(Y - X)	
(X - Y) = -00011100 ₂ = -28			

Combinational Logic

 
- outputs logical functions of inputs
- outputs appear shortly after changed inputs (propagation delay)
- no feedback loops
- no clock




Combinational Logic

Equality Comparators

1-bit comparator

 

4-bit comparator

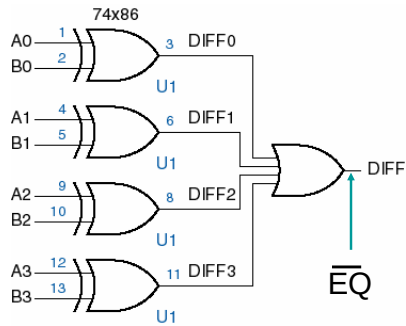

Adders

1-bit half-adder: two 1-bit inputs, output "half sum" and carry

1-bit full adder: two 1-bit inputs and carry-in, output sum and carry

Full adder truth table:




X	Y	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

S:	XY			
	00	01	11	10
0		1		1
Cin 1	1		1	


Cout:	XY			
	00	01	11	10
0			1	
Cin 1		1	1	1

$$C_{out} = XC_{in} + YC_{in} + XY$$

Full-adder circuit

  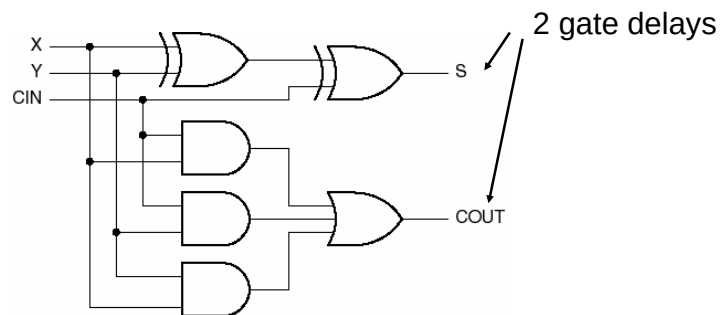


Ripple adder

 

Any limitation ?

Subtractor

Full adder

 


- No need for specific hardware
- Use full adder
- How ??? → **HOME WORK #1**

Subtraction


- Subtraction is the same as addition of the two's complement.
- The two's complement is the bit-by-bit complement plus 1.
- Therefore, $X - Y = X + \overline{Y} + 1$
 - Complement Y inputs to adder, set C_{in} to 1
 - For a borrow, set C_{in} to 0.

Encoders vs. Decoders

 

Usually binary in, 1-of-n out
e.g. in out


000	line 0 asserted
001	line 1 asserted
010	line 2 asserted
011	line 3 asserted
100	line 4 asserted
101	line 5 asserted
110	line 6 asserted
111	line 7 asserted

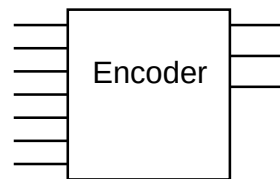


Usually 1-of-n in, binary out
e.g. out in

000	line 0 asserted
001	line 1 asserted
010	line 2 asserted
011	line 3 asserted
100	line 4 asserted
101	line 5 asserted
110	line 6 asserted
111	line 7 asserted


Binary encoders

 

 Need priority encoder in most applications




8-input priority encoder

 


Decoders

- General decoder structure

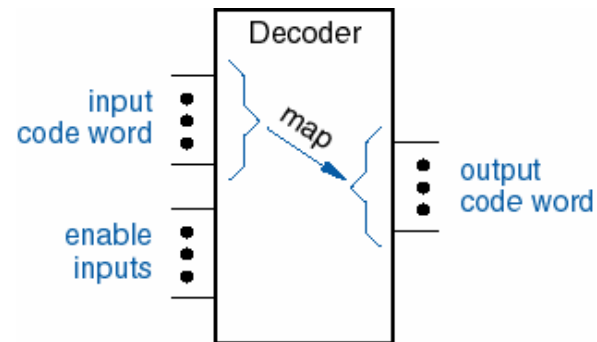


- Typically n inputs, 2^n outputs
 - 2-to-4, 3-to-8, 4-to-16, etc.

Binary 2-to-4 decoder

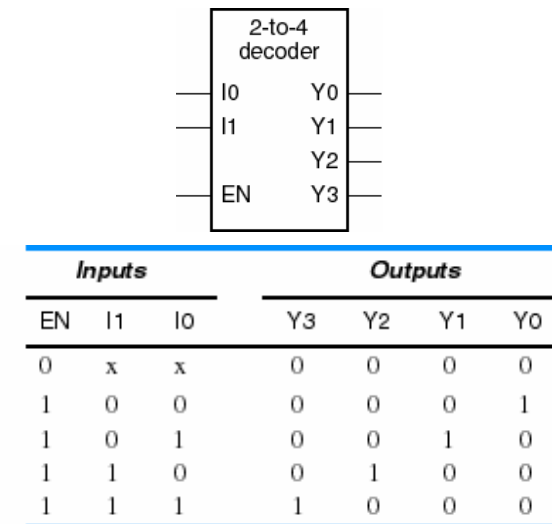


Note "x" (don't care) notation.


2-to-4-decoder logic diagram

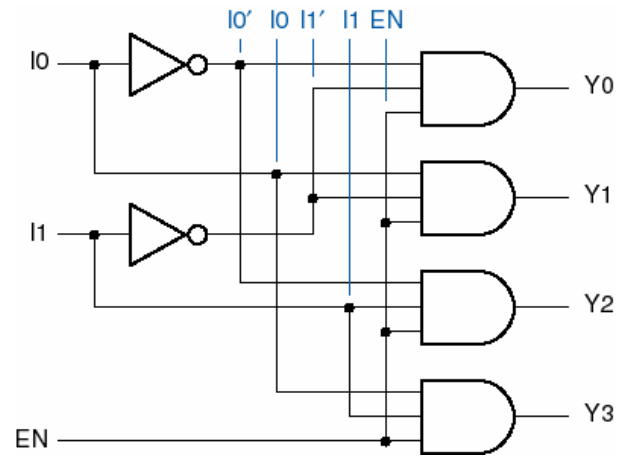


Decoder Symbol

 


Complete 74x139 Decoder

 


3-to-8 decoder

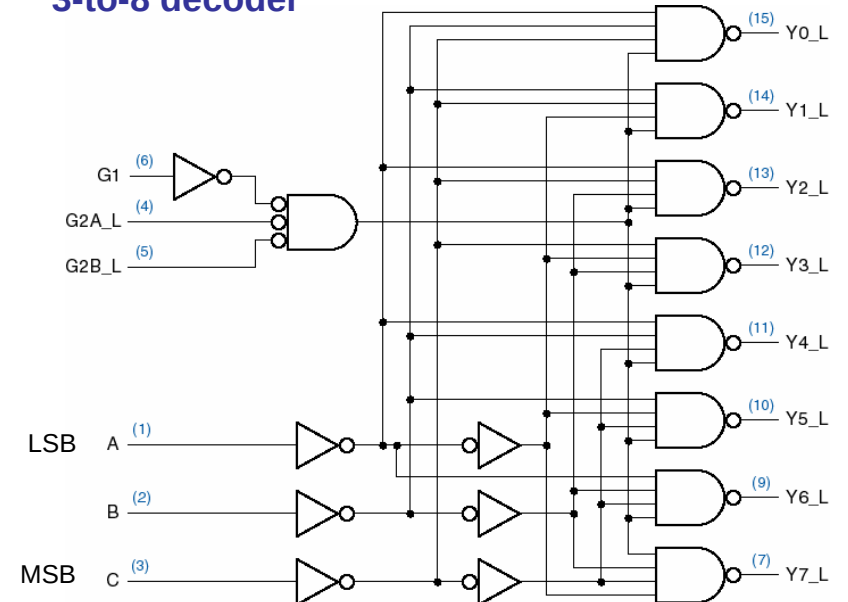

74x138 3-to-8-decoder symbol

 

Decoder cascading

 

Sequential Logic


- outputs logical functions of inputs and previous history of circuit (memory)
- after changed inputs, new outputs appear in the next clock cycle
- frequent feedback loops
- sequential circuits can be described using:

* state table

- For each current-state, specify next-states as function of inputs
- For each current-state, specify outputs as function of inputs
- Like a separate combinational problem for each state


* state diagram

graphical representation of state table

 


Clock signals

 - Very important with most sequential circuits
 - State variables change state at clock edge.



Sequential Circuit Elements


S-R Latch

 

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e


Sequential Circuit Elements

D latch

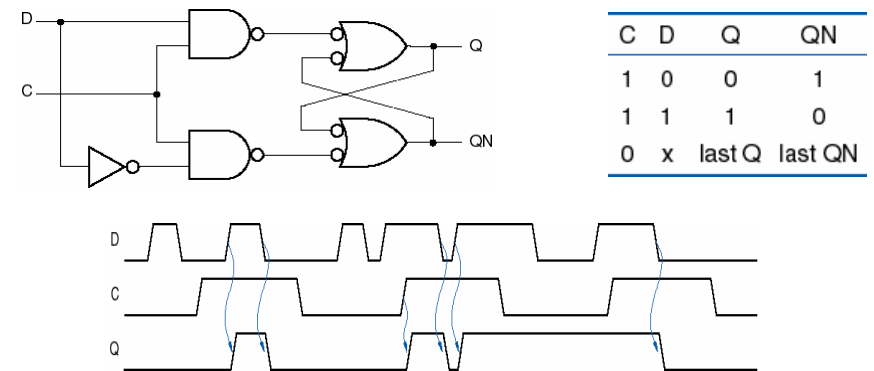

Storage Elements

 - Single Latch is 1-bit storage
- Multiple latches arranged in linear form is called **"register"**
- 2-D form of register is called **"memory"**




Storage Elements

Read/Write Memories

- a.k.a. "RAM" (Random Access Memory)
- Volatility
 - Most RAMs lose their memory when power is removed
 - NVRAM = RAM + battery
 - Or use EEPROM
- SRAM (Static RAM)
 - Memory behaves like latches or flip-flops
- DRAM (Dynamic Memory)
 - Memory lasts only for a few milliseconds
 - Must "refresh" locations by reading or writing

Storage Elements


SRAM

 

Storage Elements

SRAM operation

 - Individual bits are D latches, **not** edge-triggered D flip-flops.
 - Fewer transistors per cell.
- Implications for write operations:
 - Address must be stable before writing cell.
 - Data must be stable before ending a write.



Storage Elements

SRAM array

