

## Chapter 5 Sequential Systems

- Latches and Flip-flops
- Synchronous Counter
- Asynchronous Counter

178220 Digital Logic Design @Department of Computer Engineering KKU.

1

---

---

---

---

---

---

---

---

## Introduction

- Up to now everything has been combinational – the output at any instant of time depends only on what inputs are at the time.
- Later on of this course: *sequential systems* – systems that have memory. Thus, the output will depend not only on the present input but also on the past history – what has happened earlier.

178220 Digital Logic Design @Department of Computer Engineering KKU.

2

---

---

---

---

---


---

---

---
 
## Clock Signals

- Two versions of a clock signal are as below. In the first, the clock signal is 0 half of the time and 1 half of the time. In the second, it is 1 for a shorter part of the cycle.
- The period of the signal ( $T$  on the diagram) is the length of one cycle. The frequency is the inverse ( $1/T$ ).



178220 Digital Logic Design @Department of Computer Engineering KKU.

3

---

---

---

---

---

---

---

---

## Terminology

- **State:** what is stored in memory.
- **State table:** shows for each input combination and each state, what the output is and what the next state is – what is to be stored in memory after the next clock.
- **State diagram (or state graph):** a graphical representation of the state table.

⇒ (Finite) State Machine

178220 Digital Logic Design @Department of Computer Engineering KKU.

4

---

---

---

---


---

---

---

---

## State Table and State Diagram

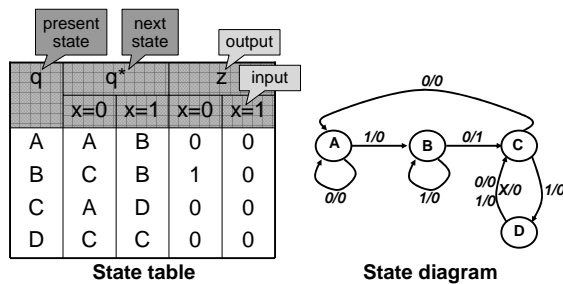

178220 Digital Logic Design @Department of Computer Engineering KKU.

5

---

---

---

---

---

---

---

---

- **The next state** is a function of the present state and the input.
- **The output** also depends on the present state (and on the input). It may change on a clock transition, but it may change where the input changes, as well.
- In **state diagram**, there must be one path from each state for each possible input combination.

178220 Digital Logic Design @Department of Computer Engineering KKU.

6

---

---

---

---

---

---

---

---

## Moore vs. Mealy Models

- **Moore model circuit (state-based)** → the outputs depend on the present state of the system but not on the inputs.
- **Mealy model circuit (input-based)** → the outputs depend on the inputs as well as the present state of the system.

178220 Digital Logic Design @Department of Computer Engineering KKU.

7

---

---

---

---

---

---

---

---

---

---

- **Moore:** A system with no input and three outputs, that represent a number from 0 to 7, such that the outputs cycle through the sequence 0 3 2 4 1 5 7 and repeat on consecutive clock inputs.
- **Mealy:** A system with two inputs,  $X_1$  and  $X_2$ , and three outputs,  $Z_1$ ,  $Z_2$  and  $Z_3$ , that represent a number from 0 to 7, such that the output counts up if  $X_1=0$  and down if  $X_1=1$  and recycles if  $X_2=0$  and saturates if  $X_2=1$ . Thus, the following output sequences might be seen:

178220 Digital Logic Design @Department of Computer Engineering KKU.

8

---

---

---

---

---

---

---

---

---

---

- $X_1=0 X_2=0$     0 1 2 3 4 5 6 7 0 1 2 3 4 5 6 7..
- $X_1=0 X_2=1$     0 1 2 3 4 5 6 7 7 7 7 7 7 7..
- $X_1=1 X_2=0$     7 6 5 4 3 2 1 0 7 6 5 4 3 2 1 0..
- $X_1=1 X_2=1$     7 6 5 4 3 2 1 0 0 0 0 0 0 0..

178220 Digital Logic Design @Department of Computer Engineering KKU.

9

---

---

---

---

---

---

---

---

---

---

## Design Process of Sequential Systems

### ■ Table 5.1 Page 338

- State table
- Timing trace
- State table with binary states
- Truth table
- K-map
- equations

---

---

---

---

---

---

---

---

---

---

---

---

## Design Process of Sequential Systems

State table

q	q*		z	
	x=0	x=1	x=0	x=1
A	A	B	0	0
B	C	B	1	0
C	A	D	0	0
D	C	C	0	0

Timing trace

clk	1	2	3	4	5	6	7	8	9	10	11	12
x	0	1	1	0	1	0	1	0	1	1		
q	A	A	B	B	C	D	C	D	C	D	C	
z	0	0	0	1	0	0	0	0	0	0	0	0

---

---

---

---

---

---

---

---

---

---

---

---

## Design Process of Sequential Systems

State assignment

q	q <sub>1</sub>	q <sub>2</sub>
A	0	0
B	0	1
C	1	0
D	1	1

State table with binary states

q <sub>1</sub>	q <sub>1</sub> *q <sub>2</sub> *		z	
	x=0	x=1	x=0	x=1
00	00	01	0	0
01	10	01	1	0
10	00	11	0	0
11	10	10	0	0

---

---

---

---

---

---

---

---

---

---


---

---

## Design Process of Sequential Systems

Truth table for system design

x	q <sub>1</sub>	q <sub>2</sub>	q <sub>1</sub> *	q <sub>2</sub> *	z
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	1	0
1	1	0	1	1	0
1	1	1	1	0	0

 

$$q^* = S + \bar{R}q$$



State assignment

178220 Digital Logic Design @Department of Computer Engineering KKU.

13

---

---

---

---

---

---

---

---

---

---

---

---

## Latches and Flip-flops

- A latch is a binary storage device, composed of two or more gates, with feedback.

The latch can store either a 0 (Q = 0 and P = 1) or a 1 (Q = 1 and P = 0)

The P output is just labelled  $\bar{Q}$

178220 Digital Logic Design @Department of Computer Engineering KKU.

14

---

---

---

---

---

---

---

---

---


---

---

---

## Latches (cont.)

 - Example: a latch constructed with 2 NORs.



The equations for this system:  
 $P = \overline{S+Q}$  and  $Q = \overline{R+P}$

Normal storage stage → both inputs inactive (S = R = 0).

$$P = \bar{Q} \quad \text{and} \quad Q = \bar{P}$$

178220 Digital Logic Design @Department of Computer Engineering KKU.

15

---

---

---

---

---

---

---

---

---

---

---

---

## Latches (cont.)

**Case 1:** If  $S=1$  and  $R=0$

$$P = \overline{(1+Q)} = \bar{1} = 0$$

$$Q = \overline{(0+0)} = \bar{0} = 1$$

**Case 2:** If  $S=0$  and  $R=1$


$$Q = \overline{(1+P)} = \bar{1} = 0$$

$$P = \overline{(0+0)} = \bar{0} = 1$$

**Case 3:** Finally, the flip-flop is not operated with both  $S$  and  $R$  active ( $=1$ ).

$$P = \overline{(1+Q)} = \bar{1} = 0$$

$$Q = \overline{(1+P)} = \bar{1} = 0$$

 

## Latches (cont.)

- D flip-flops (Delay flip-flops)
- SR flip-flops (Set/Reset flip-flops)
- T flip-flops (Toggle flip-flops)
- JK flip-flops


## D flip-flops

D	q	q*
0	0	0
0	1	0
1	0	1
1	1	1


⇒

D	q*
0	0
1	1

$$\Rightarrow q^* = D$$

 

## SR flip-flops

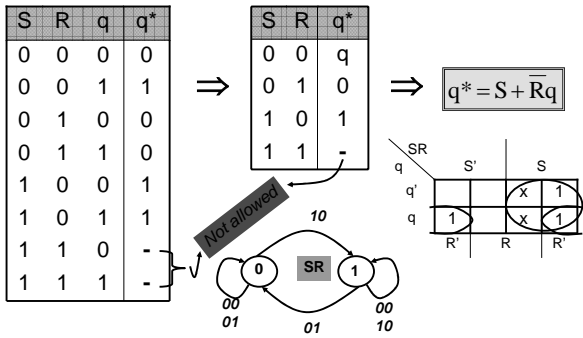

178220 Digital Logic Design @Department of Computer Engineering KKU.

19

---

---

---

---

---

---


---

---

---

---

## T flip-flops

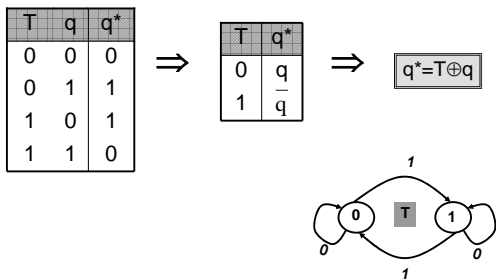

178220 Digital Logic Design @Department of Computer Engineering KKU.

20

---

---

---

---

---

---


---

---

---

---

## JK flip-flops

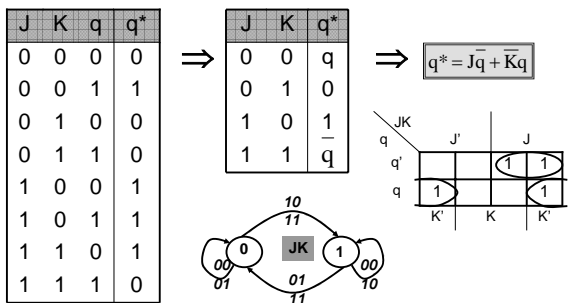

178220 Digital Logic Design @Department of Computer Engineering KKU.

21

---

---

---

---

---

---

---

---

---

---

## Latches (cont.)

- Edge-triggered
  - rising/leading edge-triggered
  - falling/trailing edge-triggered
- Level-triggered
  - high level-triggered
  - low level-triggered

---

---

---

---

---

---

---

---

## Analysis of Sequential Systems

- Figure 5.21 Page 342
  - Circuit
  - Equations
  - State table
  - Timing trace
  - Timing diagram
  - Equations  $A^*, B^*$
  - State diagram

---

---

---

---

---

---

---

---

## Flip-flop Design Techniques

x	q <sub>1</sub>	q <sub>2</sub>	q <sub>1</sub> *	q <sub>2</sub> *	z
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	1	0
1	1	0	1	1	0
1	1	1	1	0	1

Main truth table

From the truth table, it's clear that

$$z = q_1 q_2$$

We need to create the appropriate flip-flop design table to obtain a truth table for the flip-flop inputs.

q	q*	Input(s)
0	0	
0	1	
1	0	
1	1	

- D flip-flops
- JK flip-flops
- SR flip-flops
- T flip-flops

---

---

---

---

---

---

---

---



## Design with D Flip-flop

D	q*
0	0
1	1

⇒

q	q*	D
0	0	0
0	1	1
1	0	0
1	1	1

⇒

x	q <sub>1</sub>	q <sub>2</sub>	D <sub>1</sub> =q <sub>1</sub> *	D <sub>2</sub> =q <sub>2</sub> *
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	1	1
1	1	1	1	0

From the main truth table ⇒

---

---

---

---

---

---

---

---

---

---

---

---

## Design with D Flip-flop (cont.)

	x	
q <sub>1</sub> q <sub>2</sub>	0	1
00		
01		1
11		1
10		1

	x	
q <sub>1</sub> q <sub>2</sub>	0	1
00		1
01		
11		1
10		1

$$D_1 = xq_2 + xq_1$$

$$D_2 = xq_2 + \overline{xq_1}$$

---

---

---

---

---

---

---

---

---

---

---

---

## Implementation using D Flip-flops

Fig 5.26 page 352

---

---

---

---

---

---

---

---

---

---

---

---

## Design with JK Flip-flop

J	K	q*
0	0	q
0	1	0
1	0	1
1	1	$\bar{q}$

 $\Rightarrow$ 

q	q*	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

 $\Rightarrow$ 

x	q <sub>1</sub>	q <sub>2</sub>	q <sub>1</sub> *	q <sub>2</sub> *	J <sub>1</sub>	K <sub>1</sub>	J <sub>2</sub>	K <sub>2</sub>
0	0	0	0	0	0	X	0	X
0	0	1	1	0	0	X	X	1
0	1	0	0	0	X	1	0	X
0	1	1	1	0	X	1	X	1
1	0	0	0	1	0	X	1	X
1	0	1	0	1	1	X	X	1
1	1	0	1	1	X	0	1	X
1	1	1	1	0	X	0	X	0

From the main truth table  $\Rightarrow$

178220 Digital Logic Design @Department of Computer Engineering KKU.

28

---

---

---

---

---

---

---

---

---

---

---

---

## Design with JK Flip-flop (cont.)

<table border="1"> <tr><th>q1q2</th><th>0</th><th>1</th></tr> <tr><th>00</th><td></td><td></td></tr> <tr><th>01</th><td></td><td>1</td></tr> <tr><th>11</th><td>X</td><td>X</td></tr> <tr><th>10</th><td>X</td><td>X</td></tr> </table> <p>J<sub>1</sub></p>	q1q2	0	1	00			01		1	11	X	X	10	X	X	<table border="1"> <tr><th>q1q2</th><th>0</th><th>1</th></tr> <tr><th>00</th><td>X</td><td>X</td></tr> <tr><th>01</th><td>X</td><td>X</td></tr> <tr><th>11</th><td>1</td><td></td></tr> <tr><th>10</th><td>1</td><td></td></tr> </table> <p>K<sub>1</sub></p>	q1q2	0	1	00	X	X	01	X	X	11	1		10	1		<table border="1"> <tr><th>q1q2</th><th>0</th><th>1</th></tr> <tr><th>00</th><td></td><td>1</td></tr> <tr><th>01</th><td>X</td><td>X</td></tr> <tr><th>11</th><td>X</td><td>X</td></tr> <tr><th>10</th><td></td><td>1</td></tr> </table> <p>J<sub>2</sub></p>	q1q2	0	1	00		1	01	X	X	11	X	X	10		1	<table border="1"> <tr><th>q1q2</th><th>0</th><th>1</th></tr> <tr><th>00</th><td>X</td><td>X</td></tr> <tr><th>01</th><td>1</td><td>1</td></tr> <tr><th>11</th><td>1</td><td></td></tr> <tr><th>10</th><td>X</td><td>X</td></tr> </table> <p>K<sub>2</sub></p>	q1q2	0	1	00	X	X	01	1	1	11	1		10	X	X
q1q2	0	1																																																													
00																																																															
01		1																																																													
11	X	X																																																													
10	X	X																																																													
q1q2	0	1																																																													
00	X	X																																																													
01	X	X																																																													
11	1																																																														
10	1																																																														
q1q2	0	1																																																													
00		1																																																													
01	X	X																																																													
11	X	X																																																													
10		1																																																													
q1q2	0	1																																																													
00	X	X																																																													
01	1	1																																																													
11	1																																																														
10	X	X																																																													

$$J_1 = xq_2 \quad ; \quad K_1 = \bar{x}$$

$$J_2 = x \quad ; \quad K_2 = \bar{x} + q_1$$

178220 Digital Logic Design @Department of Computer Engineering KKU.

29

---

---

---

---

---

---

---

---

---

---

---

---

## Design with SR Flip-flop

S	R	q*
0	0	q
0	1	0
1	0	1
1	1	-

 $\Rightarrow$ 

q	q*	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

 $\Rightarrow$ 

x	q <sub>1</sub>	q <sub>2</sub>	q <sub>1</sub> *	q <sub>2</sub> *	S <sub>1</sub>	R <sub>1</sub>	S <sub>2</sub>	R <sub>2</sub>
0	0	0	0	0	0	X	0	X
0	0	1	1	0	0	X	0	1
0	1	0	0	0	0	1	0	X
0	1	1	1	0	0	1	0	1
1	0	0	0	1	0	X	1	0
1	0	1	0	1	1	0	0	1
1	1	0	1	1	X	0	1	0
1	1	1	1	0	X	0	X	0

From the main truth table  $\Rightarrow$

178220 Digital Logic Design @Department of Computer Engineering KKU.

30

---

---

---

---

---

---

---

---


---

---

---

---

## Design with SR Flip-flop (cont.)

 

$$S_1 = xq_2 \quad ; \quad R_1 = \overline{x}$$

$$S_2 = xq_2 \quad ; \quad R_2 = \overline{x} + q_1q_2$$

178220 Digital Logic Design @Department of Computer Engineering KKU.

31

---

---

---

---

---

---


---

---

---

---

## Design with T Flip-flop

 

178220 Digital Logic Design @Department of Computer Engineering KKU.

32

---

---

---

---

---

---


---

---

---

---

## Design with T Flip-flop (cont.)

 

178220 Digital Logic Design @Department of Computer Engineering KKU.

33

---

---

---

---

---

---

---

---

---

---

Because  $q^* = J\bar{q} + \bar{K}q$

Notice that when  $q=0$   $q^* = J \cdot 1 + \bar{K} \cdot 0 = J$   
 $\Rightarrow J = q^*$

And when  $q=1$   $q^* = J \cdot 0 + \bar{K} \cdot 1 = \bar{K}$   
 $\Rightarrow K = q^*$

---

---

---

---

---

---

---

---

---

---

## Design of Synchronous Counters

- Design a decimal or decade counter using JK flip-flops:

0, 1, 2, 3, 4, 5, 6, 7, 8, 9, 0, 1, ...

D	C	B	A	D*	C*	B*	A*
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	x	x	x	x
...	...	...	...	...	...	...	...
1	1	1	1	X	x	x	x

---

---

---

---

---

---


---

---

---

---
 
## Design of Synchronous Counters (cont.)




---

---

---

---

---

---

---

---

---

---

### Design of Synchronous Counters (cont.)

**D\***

DC	$\bar{D}$	D		
BA				$\bar{A}$
$\bar{B}$	X	X	1	$\bar{A}$
$\bar{B}$	X	X	X	A
B	1	X	X	$\bar{A}$
B	X	X	X	A
	$\bar{C}$	C	$\bar{C}$	

From the main truth table of the D\*

$J_D = CBA ; K_D = A$

**J<sub>D</sub>**

DC	$\bar{D}$	D		
BA				$\bar{A}$
$\bar{B}$	X	X	X	$\bar{A}$
$\bar{B}$	X	X	X	A
B	1	X	X	$\bar{A}$
B	X	X	X	A
	$\bar{C}$	C	$\bar{C}$	

**K<sub>D</sub>**

DC	$\bar{D}$	D		
BA				$\bar{A}$
$\bar{B}$	X	X	X	$\bar{A}$
$\bar{B}$	X	X	X	A
B	X	X	X	$\bar{A}$
B	X	X	X	A
	$\bar{C}$	C	$\bar{C}$	

178220 Digital Logic Design @Department of Computer Engineering KKU. 37

---

---

---

---

---

---

---

---

### Design of Synchronous Counters (cont.)

**C\***

DC	$\bar{D}$	D		
BA				$\bar{A}$
$\bar{B}$	1	X		$\bar{A}$
$\bar{B}$	1	X		A
B	1	X	X	$\bar{A}$
B	1	X	X	A
	$\bar{C}$	C	$\bar{C}$	

From the main truth table of the C\*

$J_C = K_C = BA$

**J<sub>C</sub>**

DC	$\bar{D}$	D		
BA				$\bar{A}$
$\bar{B}$	X	X	X	$\bar{A}$
$\bar{B}$	X	X	X	A
B	X	X	X	$\bar{A}$
B	X	X	X	A
	$\bar{C}$	C	$\bar{C}$	

**K<sub>C</sub>**

DC	$\bar{D}$	D		
BA				$\bar{A}$
$\bar{B}$	X	X	X	$\bar{A}$
$\bar{B}$	X	X	X	A
B	X	1	X	$\bar{A}$
B	X	1	X	A
	$\bar{C}$	C	$\bar{C}$	

178220 Digital Logic Design @Department of Computer Engineering KKU. 38

---

---

---

---

---

---

---

---

### Design of Synchronous Counters (cont.)

**B\***

DC	$\bar{D}$	D		
BA				$\bar{A}$
$\bar{B}$	1	1	X	$\bar{A}$
$\bar{B}$	1	1	X	A
B	1	1	X	$\bar{A}$
B	1	1	X	A
	$\bar{C}$	C	$\bar{C}$	

From the main truth table of the C\*

$J_B = \bar{D}A ; K_B = A$

**J<sub>B</sub>**

DC	$\bar{D}$	D		
BA				$\bar{A}$
$\bar{B}$	1	1	X	$\bar{A}$
$\bar{B}$	1	1	X	A
B	X	X	X	$\bar{A}$
B	X	X	X	A
	$\bar{C}$	C	$\bar{C}$	

**K<sub>B</sub>**

DC	$\bar{D}$	D		
BA				$\bar{A}$
$\bar{B}$	X	X	X	$\bar{A}$
$\bar{B}$	X	X	X	A
B	1	1	X	$\bar{A}$
B	1	1	X	A
	$\bar{C}$	C	$\bar{C}$	

178220 Digital Logic Design @Department of Computer Engineering KKU. 39

---

---

---

---

---

---

---

---

### Design of Synchronous Counters (cont.)

From the main truth table of the A\*

$J_A = K_A = 1$

178220 Digital Logic Design @Department of Computer Engineering KKU. 40

---

---

---

---

---

---

---

---

---

---

$q_1$	$q_2$	$q_3$	$q_4$	$q_1^*$	$q_2^*$	$q_3^*$	$q_4^*$
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	1	1	x	x	x	x

178220 Digital Logic Design @Dep

---

---

---

---

---

---

---

---

---

---

### Design of Asynchronous Counters

- Page 350....
- Figure 5.31(2-bit counter)&5.32(timing delay)
- Advantage:
  - Simplicity of the hardware  $\Rightarrow$  no combinational logic required
- Disadvantage:
  - Speed

178220 Digital Logic Design @Department of Computer Engineering KKU. 42

---

---

---

---

---

---

---

---

---

---

## Derivation of State tables and State Diagrams

- Consider the problem:

A system with one input  $x$  and one output  $z$  such that  $z = 1$  at a clock time iff  $x$  is currently 1 and was also 1 at the previous two clock times.

- Another way of wording this same problem is

A Mealy system with one input  $x$  and one output  $z$  such that  $z = 1$  iff  $x$  has been 1 for three consecutive clock times.

178220 Digital Logic Design @Department of Computer Engineering KKU.

43

---

---

---

---

---

---

---

---

---

---

---

---

- A sample input/output trace is

x 0 1 1 1 1 1 1 1 0 1 1 0 1 1 1 0 1  
z 0 0 0 1 1 1 1 1 0 0 0 0 0 0 1 0 0 0

- First approach:**

save the previous 2 inputs.

- Knowing them and the present input  $\rightarrow$  output.

$q_1$	$q_2$	$q_1^*q_2^*$		$z$	
		$x=0$	$x=1$	$x=0$	$x=1$
0	0	0 0	0 1	0	0
0	1	1 0	1 1	0	0
1	0	0 0	0 1	0	0
1	1	1 0	1 1	0	1

- Just discard the older input stored in memory and store the newer one plus the current input.

178220 Digital Logic Design @Department of Computer Engineering KKU.

44

---

---

---

---

---

---

---

---

---


---

---

---

- Second approach:** store in memory the number of consecutive 1's as follows:

 - A none, that is, the last input was 0
- B one
- C two or more



$q$	$q^*$		$z$	
	$x=0$	$x=1$	$x=0$	$x=1$
A	A	B	0	0
B	A	C	0	0
C	A	C	0	1

178220 Digital Logic Design @Department of Computer Engineering KKU.

45

---

---

---

---

---

---

---

---

---

---

---

---

- The second approach requires only 3 states, whereas the first requires 4. Both, however, use 2 flip-flops.
- Consider: the system produces a 1 if the input has been 1 for 25 consecutive clock times.
- Now the first approach requires to store the last 24 inputs and a state table of  $2^{24}$  rows.
- The second approach requires 25 states which can be coded with 5 flip-flops.

178220 Digital Logic Design @Department of Computer Engineering KKU.

46

---

---

---

---

---

---

---

---