

Chapter 7 Simplification of Sequential Circuits

- Tabular Method for State Reduction
- Partitions (OC and SP)
- State Reduction Using Partition
- Choosing a State Assignment

178 220 Digital Logic Design @Department of Computer Engineering KKU.

1

Two states of a sequential system are *equivalent* if, starting in either state, any one input produces the same output and equivalent next states.

- If two states are equivalent, we can remove one of them and have a system with fewer states.
- Usually, systems with fewer states are less expensive to implement.

178 220 Digital Logic Design @Department of Computer Engineering KKU.

2

- Occasionally, we can tell states are equivalent by just inspecting the state table.

q	q*		z	
	x=0	x=1	x=0	x=1
A	C	B	0	0
B	E	D	0	0
C	A	D	0	1
D	A	B	0	1
E	A	B	0	1

A state table

(Back to the example)

q	q*		z	
	x=0	x=1	x=0	x=1
A	C	B	0	0
B	E	D	0	0
C	A	D	0	1
D	A	B	0	1

Reduced state table

178 220 Digital Logic Design @Department of Computer Engineering KKU.

3

Tabular Method for State Reduction

- A technique using a chart with one square for each possible pairing of states.
- Enter in that square
 - ❶ an X if those states cannot be equivalent because the outputs are different,
 - ❷ a \checkmark if the states are equivalent (because they have the same output and go to the same state or to each other for each input), and
 - ❸ otherwise the conditions that must be met for those two states to be equivalent.

178 220 Digital Logic Design @Department of Computer Engineering KKU.


4

For example (from the previous state table):

In the AB square, in order for states A and B to be equivalent, they must have the same output for both $x=0$ and $x=1$ (which they do) and must go to equivalent states. Thus C must be equivalent to E and B must be equivalent to D.


Those squares contain X because states A and B have a 0 output for $x=1$ and states C,D and E have a 1 output.

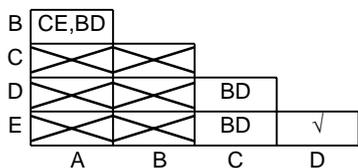Finally, the DE square contains \checkmark since both states have the same output and the next state for each input.



178 220 Digital Logic Design @Department of Computer Engineering KKU.


5

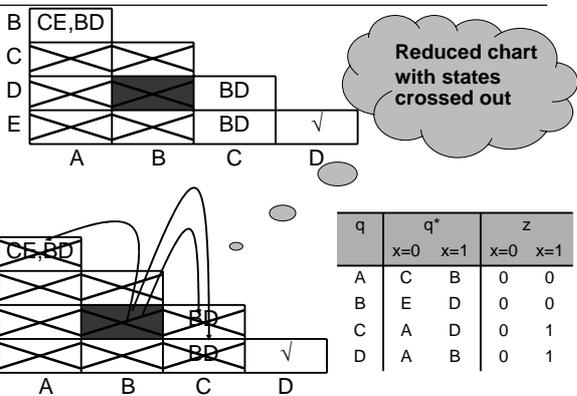

178 220 Digital Logic Design @Department of Computer Engineering KKU.

6

Example

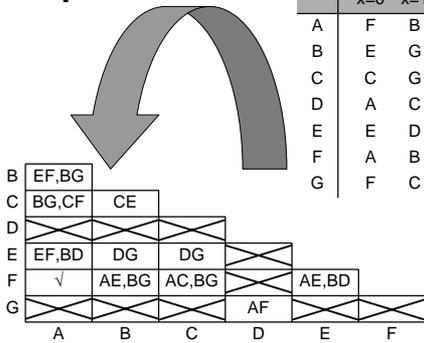


q	q*		z	
	x=0	x=1	x=0	x=1
A	F	B	0	0
B	E	G	0	0
C	C	G	0	0
D	A	C	1	1
E	E	D	0	0
F	A	B	0	0
G	F	C	1	1

178 220 Digital Logic Design @Department of Computer Engineering KKU.

7

Example (CONT.)

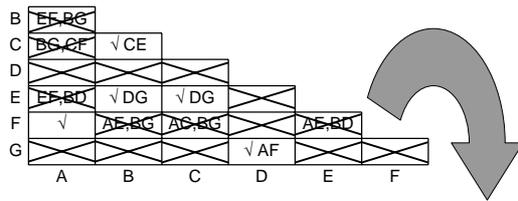

q	q*		z	
	x=0	x=1	x=0	x=1
A-F	A	B	0	0
B-C-E	B	D	0	0
D-G	A	C	1	1

178 220 Digital Logic Design @Department of Computer Engineering KKU.

8

Partitions

A *partition* on the state of a system is a grouping of the states of that system into one or more blocks. Each state must be in one and only one block.

- For a system with 4 states; A, B, C, and D, the complete list of partition is:

$$\begin{aligned}
 P_0 &= (A)(B)(C)(D) & P_4 &= (A)(BC)(D) & P_7 &= (AB)(CD) & P_{11} &= (ABD)(C) \\
 P_1 &= (AB)(C)(D) & P_5 &= (A)(BD)(C) & P_8 &= (AC)(BD) & P_{12} &= (ACD)(B) \\
 P_2 &= (AC)(B)(D) & P_6 &= (A)(B)(CD) & P_9 &= (AD)(BC) & P_{13} &= (A)(BCD) \\
 P_3 &= (AD)(B)(C) & & & P_{10} &= (ABC)(D) & P_N &= (ABCD)
 \end{aligned}$$

178 220 Digital Logic Design @Department of Computer Engineering KKU.

9

Output consistent (OC)

- Another useful class of partitions for which all of the states in each block have the same output for each of the inputs.

- $P_0 (= (A)(B)(C)(D))$ is always OC.

$$P_2 = (AC)(B)(D)$$

$$P_5 = (A)(BD)(C)$$

$$P_8 = (AC)(BD)$$



q	q*		z
	x=0	x=1	
A	C	A	1
B	D	B	0
C	A	B	1
D	B	A	0

- Knowing the block of an OC partition and the input is enough info to determine the output (without having to know which state within a block).

178 220 Digital Logic Design @Department of Computer Engineering KKU.

13

Substitution Property (SP) Partition

- For SP partitions, knowing the block of the partition and the input is enough info to determine the block of the next state.

- $P_N (= (ABCD))$ is always SP since all states are in the same block.

- $P_0 (= (A)(B)(C)(D))$ is always SP since knowing the block is the same as knowing the state.

q	q*		z
	x=0	x=1	
A	C	A	1
B	D	B	0
C	A	B	1
D	B	A	0

$$P_7 = (AB)(CD)$$

$$P_9 = (AD)(BC)$$

178 220 Digital Logic Design @Department of Computer Engineering KKU.

14

- If a partition other than P_0 is both SP and OC, then the system can be reduced to one having just one state for each block of that partition.

- That should be obvious since knowing the input and the block of the partition is all we need to know to determine the output, since it is **OC**, and to determine the next state, since it is **SP**.

178 220 Digital Logic Design @Department of Computer Engineering KKU.

15

Properties of Partitions

Greater than or equal (\geq)

$P_a \geq P_b$ iff all states in the same block of P_b are also in the same block of P_a .

$$P_{10} = (ABC)(D) \geq P_2 = (AC)(B)(D)$$

178 220 Digital Logic Design @Department of Computer Engineering KKU.

16

Properties of Partitions (cont.)

Product

Two states are in the same block of the product P_c iff they are in the same block of both P_a and P_b .

$$P_{12}P_{13} = \{(ACD)(B)\}\{(A)(BCD)\} = (A)(B)(CD) = P_6$$

$$P_a P_0 = P_0 \text{ and } P_a P_N = P_a$$

$$P_0 = (A)(B)(C)(D)$$

$$P_N = (ABCD)$$

178 220 Digital Logic Design @Department of Computer Engineering KKU.

17

Properties of Partitions (cont.)

Sum

Two states are in the same block of the sum P_d if they are in the same block of either P_a or P_b or both.

$$P_2 + P_5 = \{(AC)(B)(D)\} + \{(A)(BD)(C)\} \\ = P_8 = (AC)(BD)$$

$$P_a + P_0 = P_a \text{ and } P_a + P_N = P_N$$

$$P_0 = (A)(B)(C)(D)$$

$$P_N = (ABCD)$$

178 220 Digital Logic Design @Department of Computer Engineering KKU.

18

Finding SP Partitions

- Step 1: สำหรับ state แต่ละคู่ หา SP Partition ที่เล็กที่สุดที่ทำให้ states คู่ นั้นอยู่ในกลุ่มเดียวกัน

q	q*			⇒	P _i
	x=0	x=1			
A	C	D	(AB) → √		P₁ = (AB)(C)(D)
B	C	D	(AC) → (BC), (BC) → ok		P₂ = (ABC)(D)
C	B	D	(AD) → √		P₃ = (AD)(B)(C)
D	C	A	(BC) → √		P₄ = (A)(BC)(D)
			(BD) → (AD) → (ABD)		P₅ = (ABD)(C)
			(CD) → (BC), (AD)		P_N

Step 1 produces 5 SP partitions.

178 220 Digital Logic Design @Department of Computer Engineering KKU.

19

Finding SP Partitions (cont.)

- Step 2: หาผลรวมของ SP Partitions ทั้งหมดจาก step 1 และทำซ้ำกับ SP Partitions ใหม่ที่เกิดขึ้นด้วย

$P_1 + P_2 = (ABC)(D) ⇒ P_2$	<i>not needed</i>	<div style="border: 1px solid black; padding: 5px; display: inline-block;"> Step 2 here really only requires 3 sums. </div>
$P_1 + P_3 = (ABD)(C) ⇒ P_5$		
$P_1 + P_4 = (ABC)(D) ⇒ P_2$		
$P_1 + P_5 = (ABD)(C) ⇒ P_5$		
$P_2 + P_3 ⇒ P_N$	<i>not needed</i>	
$P_2 + P_4 = (ABC)(D) ⇒ P_2$	<i>not needed</i>	
$P_2 + P_5 ⇒ P_N$	<i>not needed</i>	
$P_3 + P_4 = (ABC)(D) ⇒ P_6 = (AD)(BC)$	<i>only one new SP from step 2</i>	
$P_3 + P_5 = (ABD)(C) ⇒ P_5$	<i>not needed</i>	
$P_4 + P_5 ⇒ P_N$	<i>not needed</i>	

178 220 Digital Logic Design @Department of Computer Engineering KKU.

20

Blues are two-block and thus never produce anything new!

Example SP-1

q	q*			⇒	P _i
	x=0	x=1			
A	C	A	(AB) → (CD)		(AB)(CD) = P₁
B	D	B	(AC) → (AB) → (CD)		(ABCD) = P_N
C	A	B	(AD) → (BC)		(AD)(BC) = P₂
D	B	A	(BC) → (AD)		(AD)(BC) = P₂
			(BD) → (AB)		= P_N
			(CD) → (AB)		(AB)(CD) = P₁

Only step 1! No need for step 2.

178 220 Digital Logic Design @Department of Computer Engineering KKU.

21

Example SP-2

Step 1:

q	q*		z		
	x=0	x=1			
A	C	D	0	(AE) → √	⇒(AE)(B)(C)(D) = P ₃
B	D	A	0	(BC) → (ADE)	⇒P ₂
C	E	D	0	(BD) → √	⇒(A)(BD)(C)(E) = P ₄
D	B	A	1	(BE) → (ACD) → (BCE)	⇒P _N
E	C	D	1	(CD) → (BE)(AD) → (BC)	⇒P _N
				(CE) → √	⇒(A)(B)(CE)(D) = P ₅
				(DE) → (BC)(AD) → (ADE)	⇒P ₂

Step 1 produces 5 SP partitions.

178 220 Digital Logic Design @Department of Computer Engineering KKU.

22

Example SP-2 (cont.)

Step 2:

From step 1:

- P₁=(ACE)(B)(D)
- P₂=(ADE)(BC) → 2-block partition (not needed to produce new SP)
- P₃=(AE)(B)(C)(D)
- P₄=(A)(BD)(C)(E)
- P₅=(A)(B)(CE)(D)

P₁+P₄= (ACE)(BD) = P₆ → 2-block partition (not needed)
 P₃+P₄= (AE)(BD)(C) = P₇
 P₃+P₅= (ACE)(B)(D) = P₁
 P₄+P₅= (A)(BD)(CE) = P₈
 Now add pairs of these new partitions:
 P₇+P₈= (ACE)(BD) = P₆
 If there were new partitions of more than 2 blocks → repeat!

From this example, there are 8 nontrivial SP partitions, of which two are 2-block and none are OC.

178 220 Digital Logic Design @Department of Computer Engineering KKU.

23

State reduction using partitions

Any partition that is both **OC** and **SP** can be used to reduce the system to one with one state for each block of that partition.

Just as there is always a unique largest SP partition (P_N), there is always a unique largest OC SP partition. That is the one with the fewest blocks and thus corresponds to the reduced system with the fewest number of states.

(It is possible that P_N is OC; but that is a combinational system, where the output does not depend on the state.)


178 220 Digital Logic Design @Department of Computer Engineering KKU.

24

Example OC/SP-2 (cont.)

q	q*		z
	x=0	x=1	
A	C	D	0
B	D	A	1
C	E	D	0
D	B	A	1
E	C	D	0

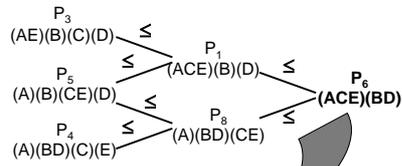In (b), P_1, P_3, P_4, P_5, P_6 and P_8 are the only OC partitions. Since



q	q*		z
	x=0	x=1	
A	A	B	0
B	B	A	1

178 220 Digital Logic Design @Department of Computer Engineering KKU.

28

Choosing a state assignment

- 2 states $\Rightarrow P_0$
- 3-4 states $\Rightarrow 3$ state assignments
- 5 states $\Rightarrow 140$ state assignments
- 6 states $\Rightarrow 420$ state assignments
- 7-8 states $\Rightarrow 840$ state assignments
- ...

178 220 Digital Logic Design @Department of Computer Engineering KKU.

29

Example

q	q*		Z
	x=0	x=1	
A	B	C	0
B	A	D	1
C	A	D	0
D	B	C	1

SP Partitions: $P_1 = (AB)(CD) \Rightarrow$ can be used
 $P_2 = (AD)(B)(C)$
 $P_3 = (A)(BC)(D)$
 $P_2 + P_3 = P_4 = (AD)(BC) \Rightarrow$ can be used

OC: $(AC)(BD)$

178 220 Digital Logic Design @Department of Computer Engineering KKU.

30

Example (cont.)

q	q ₁	q ₂
A	0	0
B	0	1
C	1	1
D	1	0

q	q ₁	q ₂
A	0	0
B	0	1
C	1	0
D	1	1

q	q ₁	q ₂
A	0	0
B	1	1
C	0	1
D	1	0

$$q_1 \leftarrow P1 (AB)(CD)$$

$$q_2 \leftarrow P4 (AD)(BC)$$

$$q_1 \leftarrow P1 (AB)(CD)$$

$$q_2 \leftarrow OC (AC)(BD)$$

$$q_1 \leftarrow OC (AC)(BD)$$

$$q_2 \leftarrow P4 (AD)(BC)$$

$$Z = q_1'q_2 + q_1q_2'$$

$$D_1 = x$$

$$D_2 = q_2'$$

$$Z = q_2'$$

$$D_1 = x$$

$$D_2 = x'q_1'q_2' + x'q_1q_2 + xq_1'q_2 + xq_1q_2'$$

$$Z = q_1$$

$$D_1 = x'q_2' + xq_2$$

$$D_2 = q_2'$$

178 220 Digital Logic Design @Department of Computer Engineering KRU.

31

Conclusions

- The choice of state assignment is more an art than a science.
- Use two-block SP partitions when possible
- When run out of those, OC partition
- And the grouping suggested by other SP partitions (if there are any).

178 220 Digital Logic Design @Department of Computer Engineering KRU.

32
